

Student Id:

Name:

Signature:

CSE 221 - Principles of Logic Design - 2021 Fall

Homework3

You will use a “key” to solve the questions in this homework. The key is the number formed by the last two digits of your student id. If your key is less than 20, add 20 to it! (So for example, if your student id was 20100702047 your key would be “47”; if your student id was 20100702008 your key would be “28”.) We will assume that the key is 47 while explaining the questions (you should replace it with your own key).

So, first write down your id and key: **Student Id:** **Key:**

1) Some terms are listed in the table below.

Term #	Term	Term #	Term	Term #	Term	Term #	Term
0 (t_0)	xyz	4	xy	8	$x' + y' + z$	12	$x + y$
1	$x'yz$	5	xz	9	$x + y + z'$	13	$x + z$
2	xyz'	6	yz	10	$x + y' + z'$	14	$y + z$
3	$x'yz'$	7	$x'y$	11	$x + y + z$	15	$x + y'$

$m = \text{key} \bmod 3$ ($m=47 \bmod 3=2$). Find your m . $m = \dots \bmod 3 = \dots$

$n = \text{key} \bmod 5$ ($n=47 \bmod 5=2$). Find your n . $n = \dots \bmod 5 = \dots$

$p = \text{key} \bmod 8$ ($p=47 \bmod 8=7$). Find your p . $p = \dots \bmod 8 = \dots$

$F_1 = t_m + t_n + t_p$ ($F_1 = t_2 + t_2 + t_7 = xyz' + x'y$)

Find your F_1 . $F_1 = t_{\dots} + t_{\dots} + t_{\dots} =$

Using algebraic methods, find the minterms of this function; then list the minterms in minterm shorthand form ($\Sigma(\dots)$) and using any method write the function in product of maxterms form ($F = (x + y' + z) \wedge (x + y' + z') \wedge \dots$).

2) Use m, n and p from question 1.

m = key mod 3 ($m=2$). Write down your m.

n = key mod 5 ($n=2$). Write down your n.

p = key mod 8 ($p=7$). Write down your p.

m = x = m+7 = ($x=9$)

n = y = n+4 = ($y=6$)

p = z = p+5 = ($z=12$)

$F_2(A, B, C, D) = \Sigma(m, n, p, x, y, z)$ ($F = \Sigma(2, 2, 7, 9, 6, 12) = \Sigma(2, 6, 7, 9, 12)$).

Write down your F. $F = \Sigma(\quad , \quad , \quad , \quad , \quad , \quad) = \Sigma(\quad)$

Using the map method, simplify F to SOP form

Write F in NAND-NAND form

Draw its circuit with NAND gates

Using the map method, simplify F to POS form

Write F in NOR-NOR form

Draw its circuit with NOR gates

3) Use m from question 1; $m = \text{key} \bmod 3$ ($m=2$). Write down your m. $m =$

Select one of the three functions below (F_m is your function). (F_2 is my function)

$$F_0 = AB'CD' + A'BCD' + AB'C'D + A'BC'D$$

$$F_1 = ABC'D + ABCD'$$

$$F_2 = A'D + B'C'D + BCD + AB'CD' + ABC'D'$$

Implement F_m with XOR and AND gates.

4) Write down your function in question 1. ($F_1 = xyz' + x'y$)

$F_1 =$

Implement F_1 using a high-active 3x8 Decoder.

Implement F_1 using a low-active 3x8 Decoder.


Implement F_1 using an 8x1 Multiplexer.

Implement F_1 using a 4x1 Multiplexer.

5) Write down your terms from question 1: t_m : t_n : t_p :

F_5 is implemented with a 4x1 MUX (with a low-active enable input) as seen on the right.

Find F_5 .

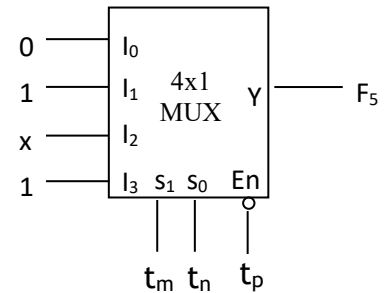


6) $r = 10 + \text{key} \bmod 20$ ($r = 10 + 47 \bmod 20 = 10 + 7 = 17$).

Find your r . $r = 10 + \dots \bmod 20 = 10 + \dots = \dots$

Design the circuit on the right. It has a 5-bit input A ($A_4A_3A_2A_1A_0$) and two outputs x and y . If A is larger than your number r , x should be equal to 1; if it is smaller, y should be 1 and otherwise both outputs should be 0.

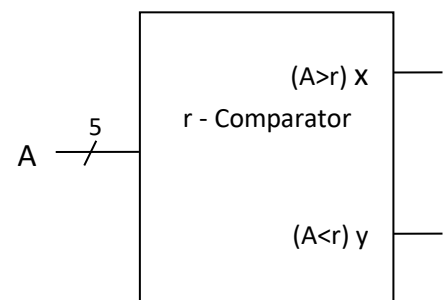Don't draw the circuit; writing the equations of x and y is enough.




7) $s = 2 + \text{key} \bmod 4$ ($s=2+47 \bmod 4=2+3=5$).

Find your s . $s = 2 + \dots \bmod 4 = 2 + \dots = \dots$

Design the circuit on the right. It has a 3-bit input A ($A_2A_1A_0$) and four outputs. The circuit should add your number “ s ” to A .

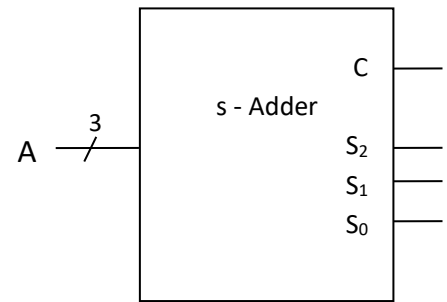Use minimum number of half-adders and full-adders (you should find the optimal design; so for example if a half-adder is enough for some part of the circuit you should not put a full-adder instead).



8) $t = 3 + 2 * (\text{key} \bmod 3)$ ($t=3+2*(47 \bmod 3)=3+2*2=7$).

Find your t . $t = 3 + 2 * (\dots \bmod 3) = 3 + 2 * \dots = \dots$

Design the circuit on the right. It has a 3-bit input A ($A_2A_1A_0$) and n outputs ($b_0 b_1 \dots b_{n-1}$). The circuit should multiply A with your number “ t ”.

Use at most two binary adders (of any size).

